


VLSI Summer School Project Documentation 2025

Group Member:Krrish Kumar(23EE10033)

Kushagra Poonia(23EE10036)



Assignment 3: Single-ended OTA

- Circuit Diagram:

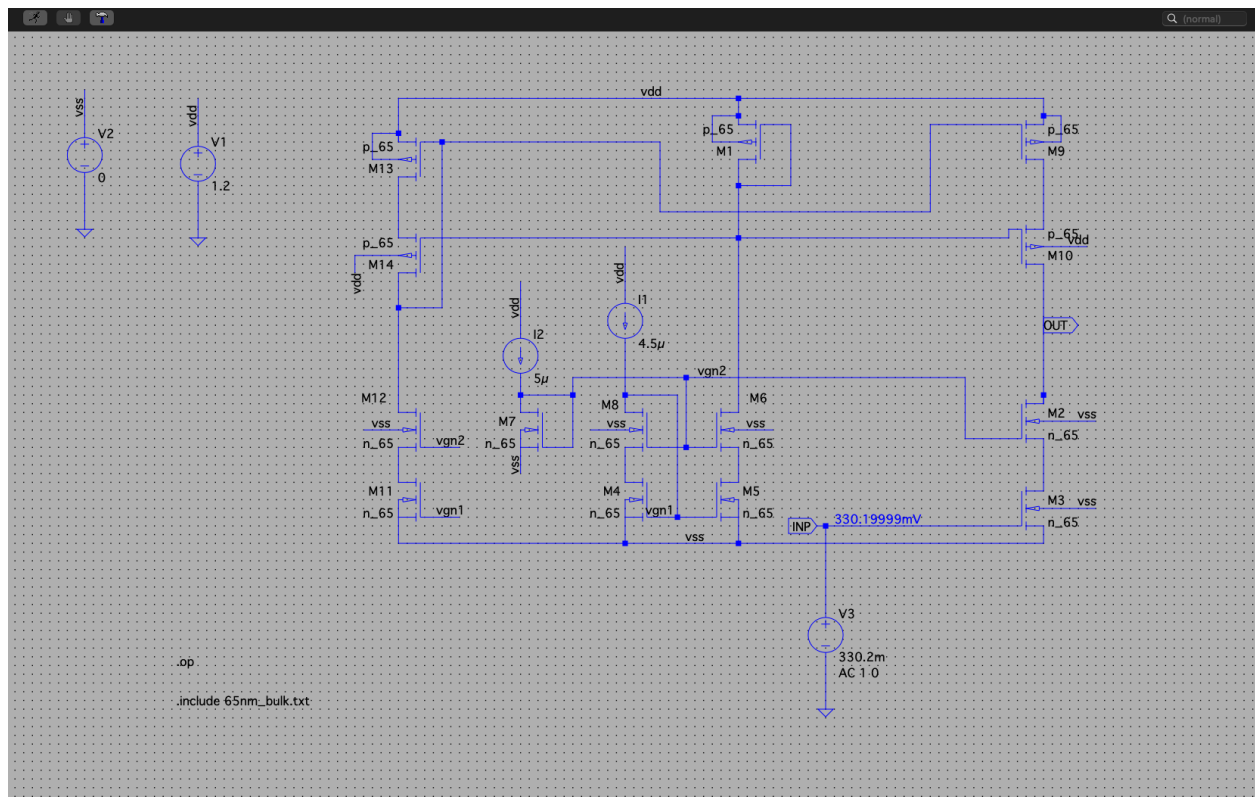

Assignment 3: Single-ended OTA

i)DC analysis:

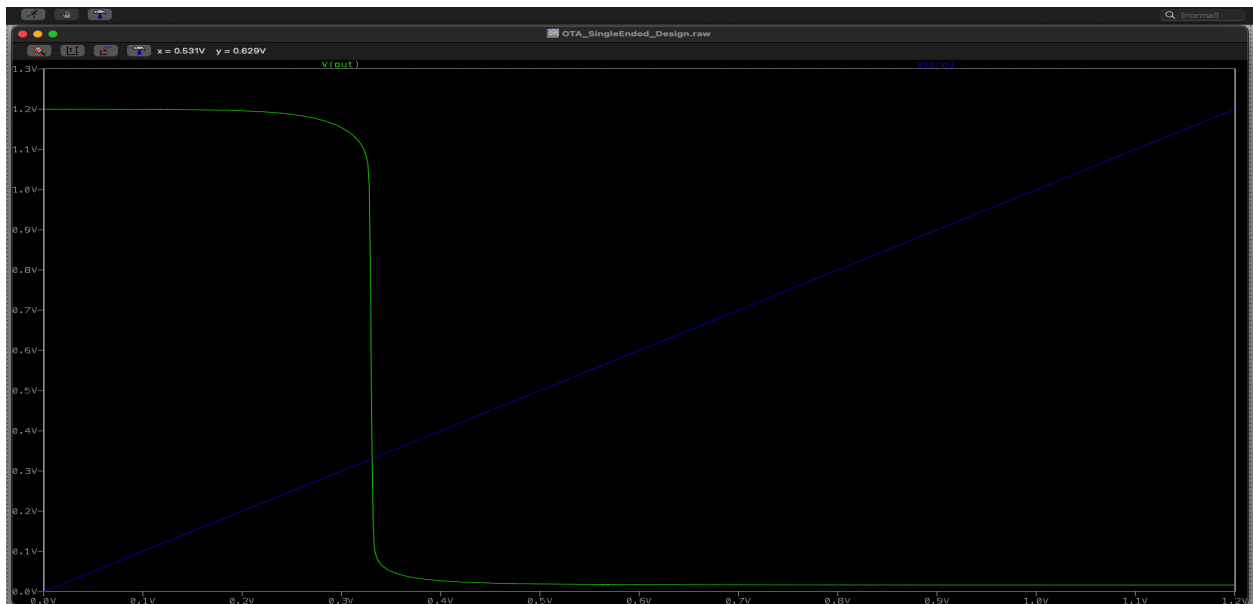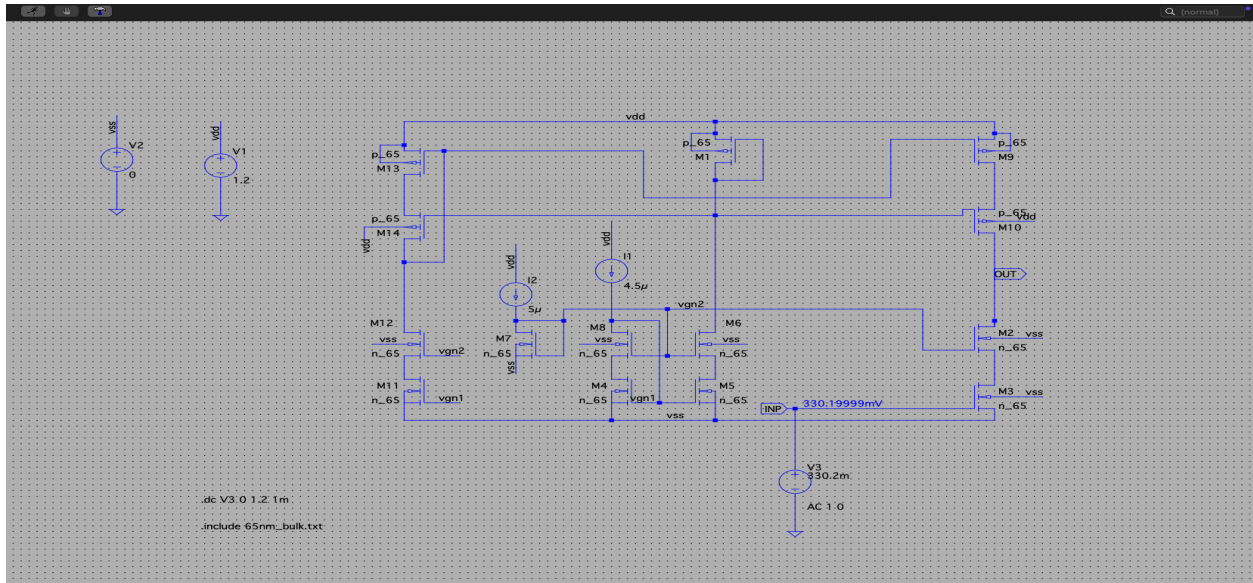


V_{in} :330.2mV for high gain circuit behaviour

Assignment 3: Single-ended OTA

ii) AC analysis:

- At $I_1 = 5\mu\text{A}$:

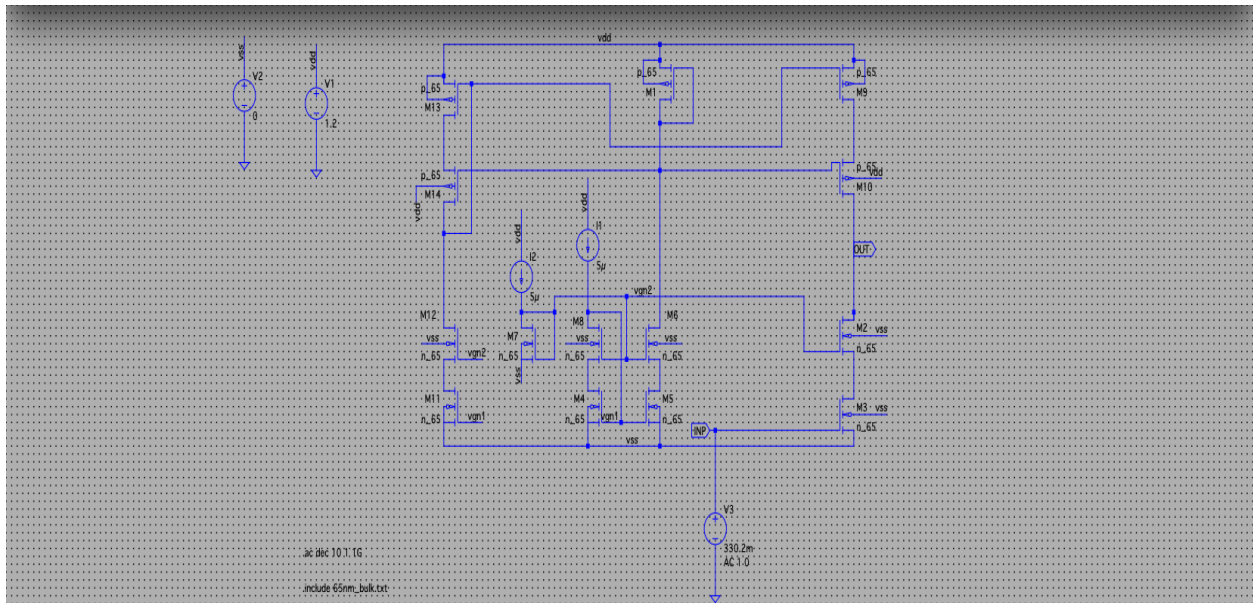



- Gain(dB) = 14dB

Assignment 3: Single-ended OTA

ii) AC analysis:

- At $I_1 = 4.8\mu\text{A}$

FOR GAIN(2x)

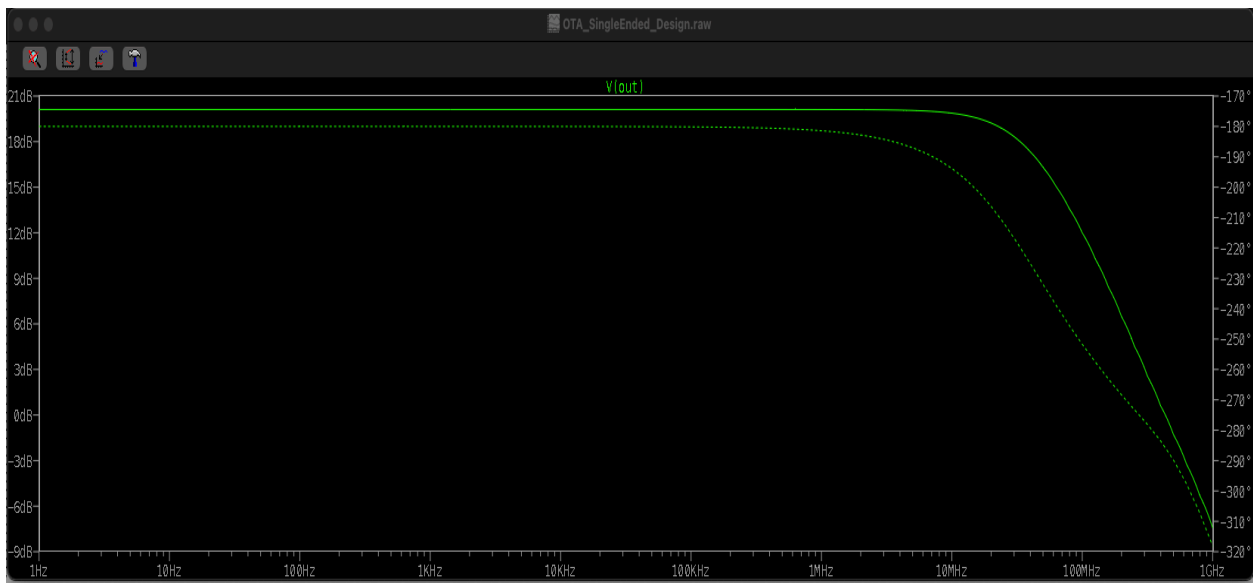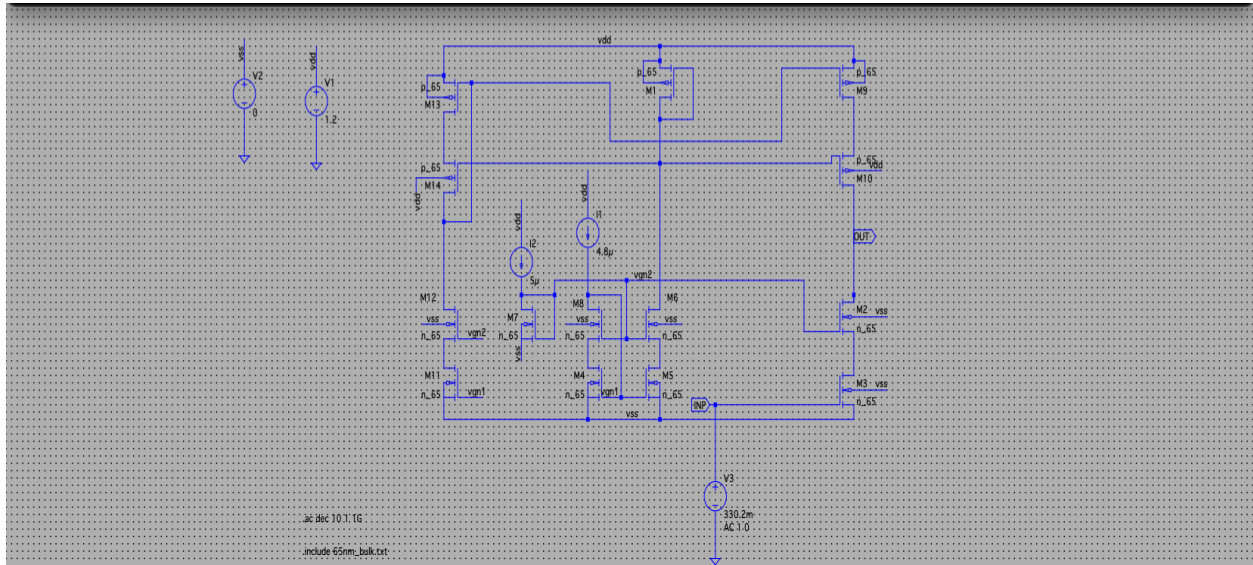



- Gain(dB)= 20dB

Assignment 3: Single-ended OTA

ii) AC analysis:

- At $I_1 = 4.5\mu\text{A}$



FOR GAIN(50x)

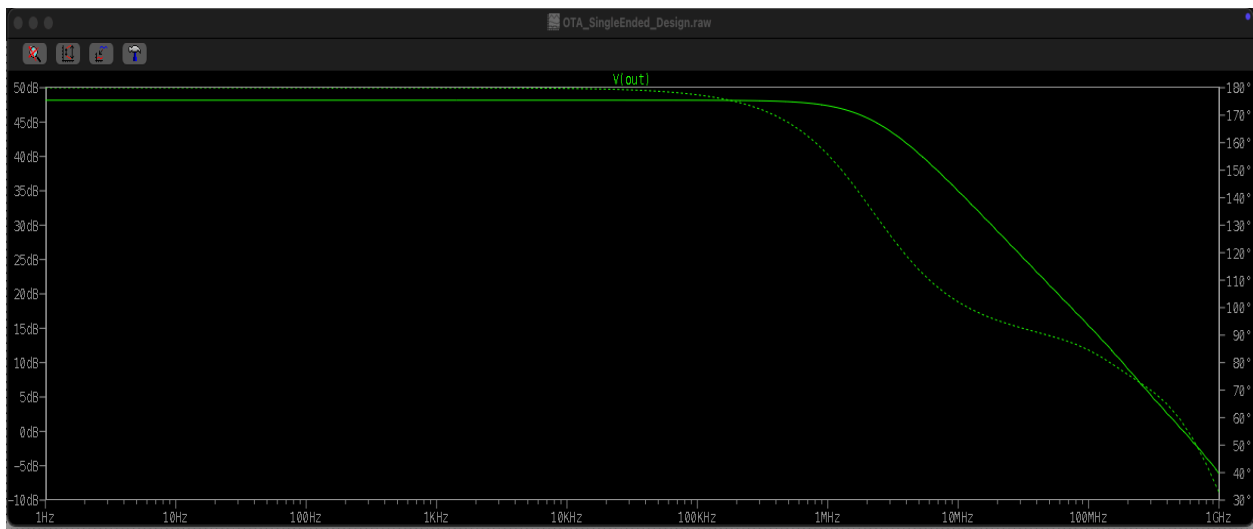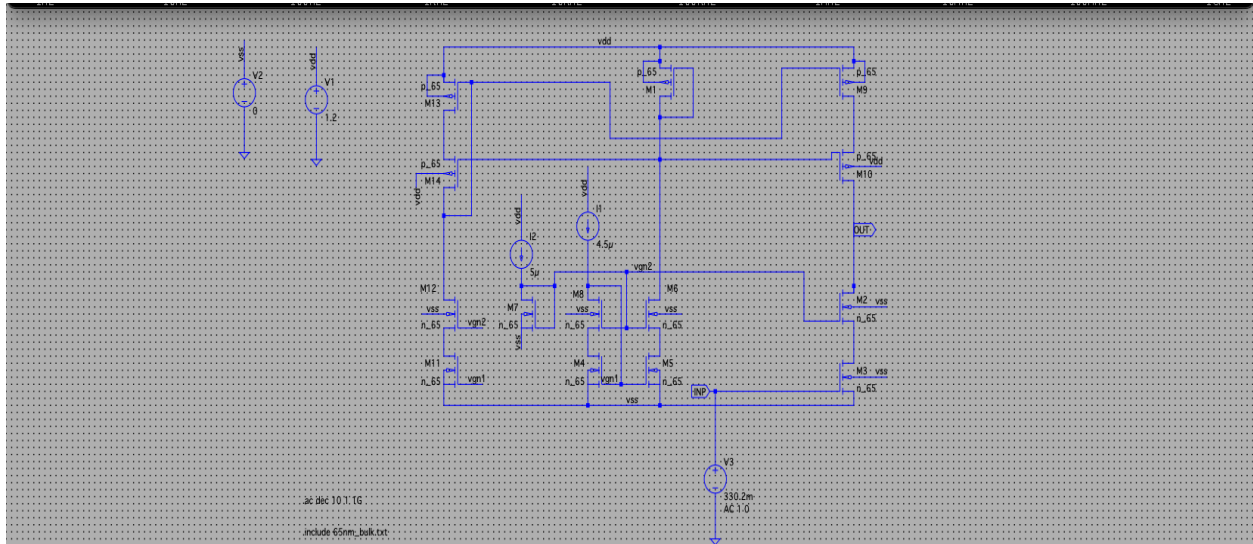

- Gain(dB) = 48dB

Assignment 3: Single-ended OTA

iii) Transient analysis:

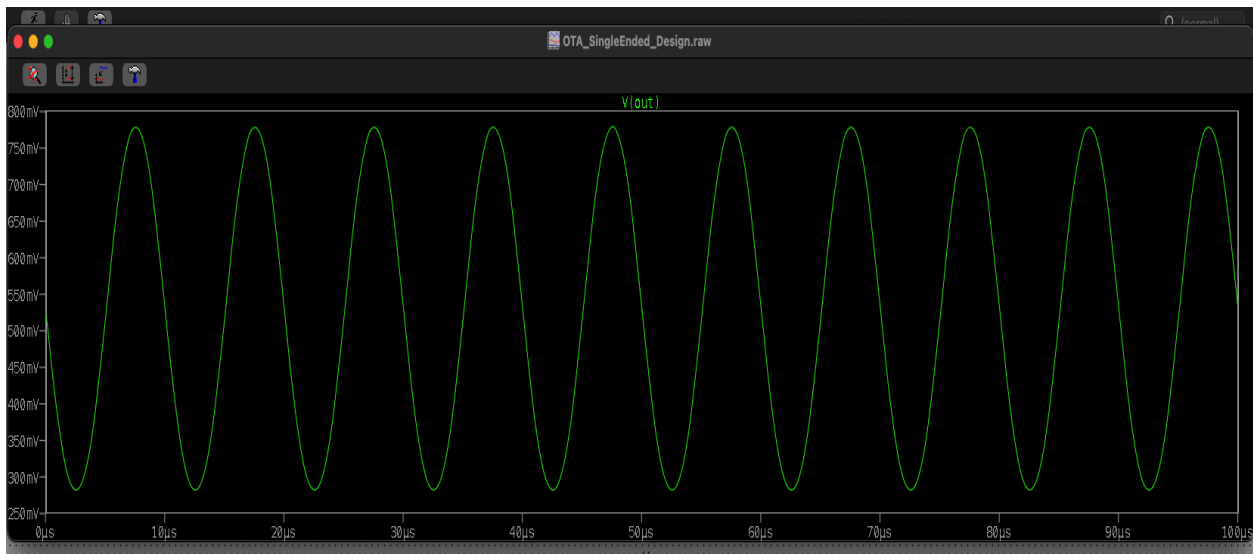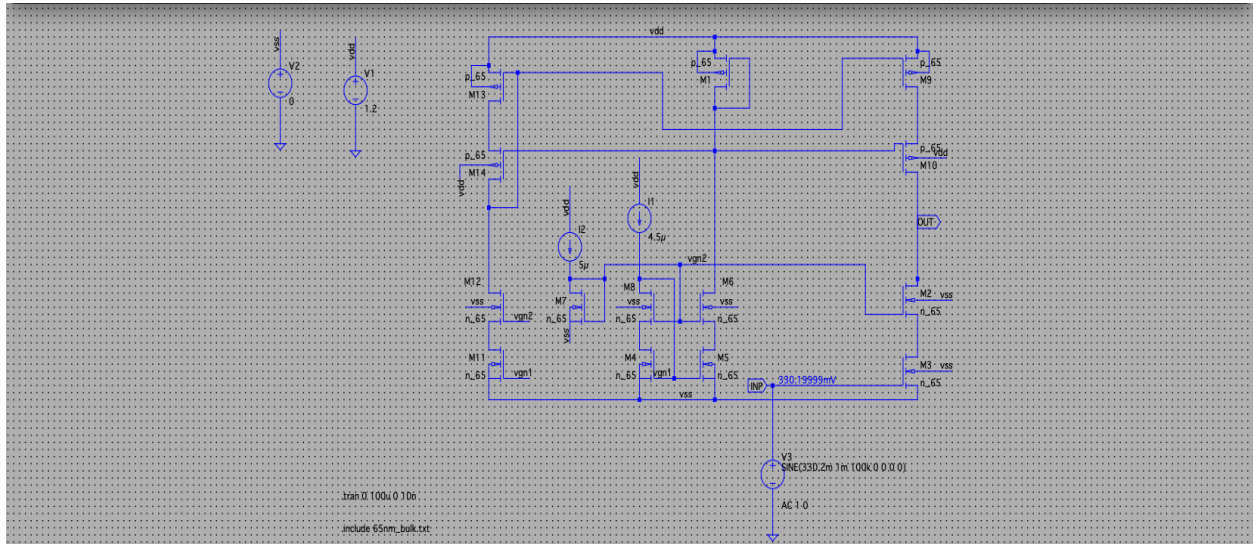

$V_{out}(\text{green}): \text{pk-pk} \sim 500\text{mV}$