


VLSI Summer School Project Documentation 2025

Group Member:Krrish Kumar(23EE10033) Kushagra Poonia(23EE10036)

Assignment 5: Differential amplifier




Part A:

- Circuit Diagram:

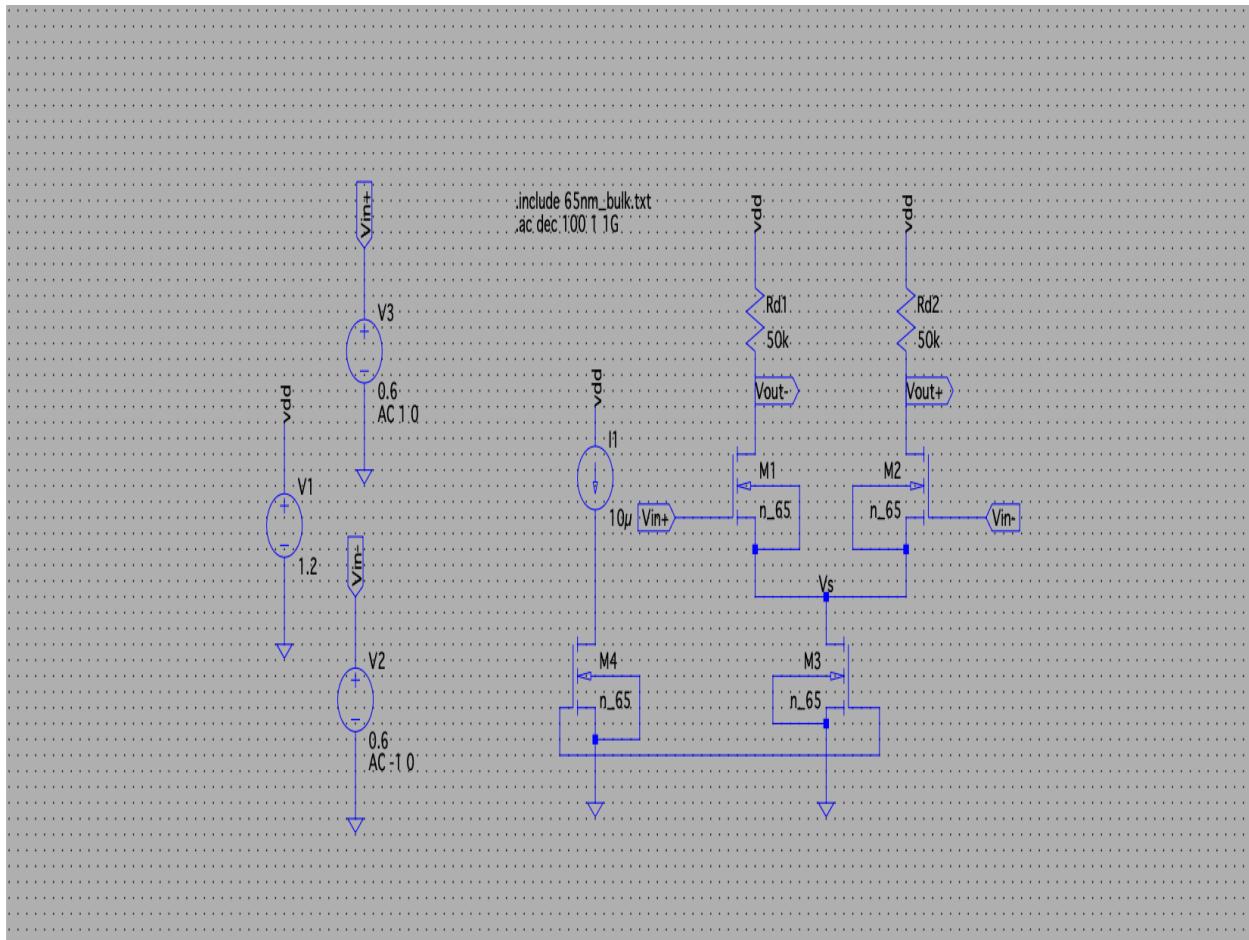

Assignment 5: Differential amplifier

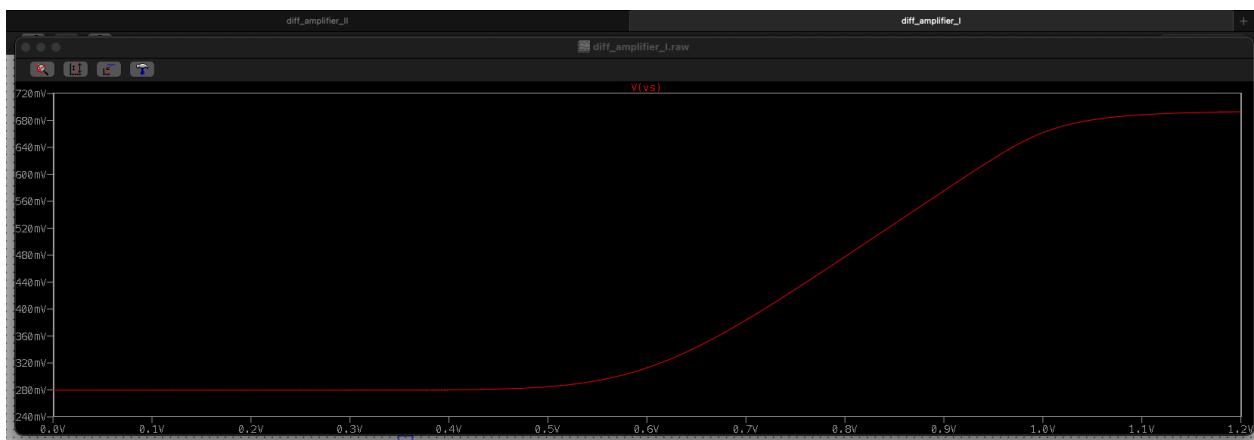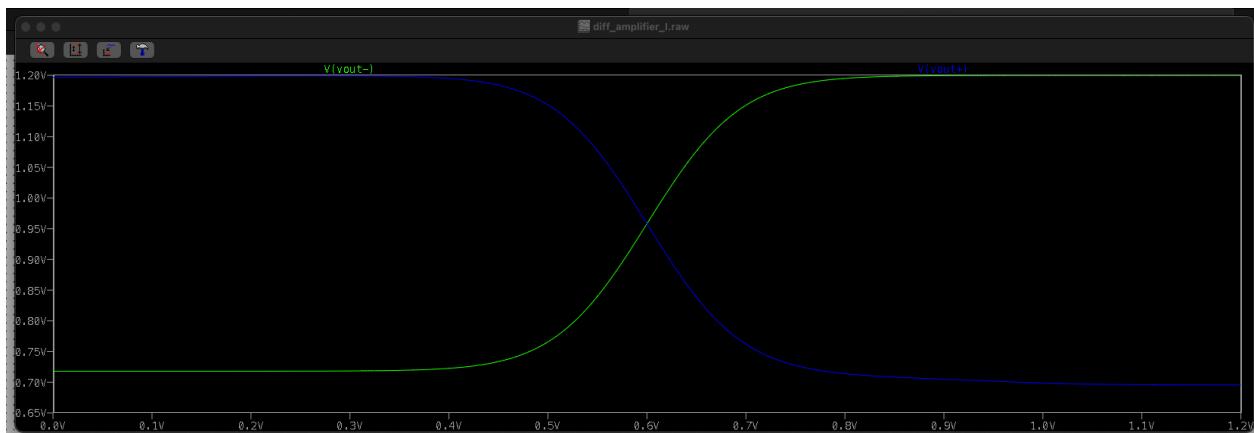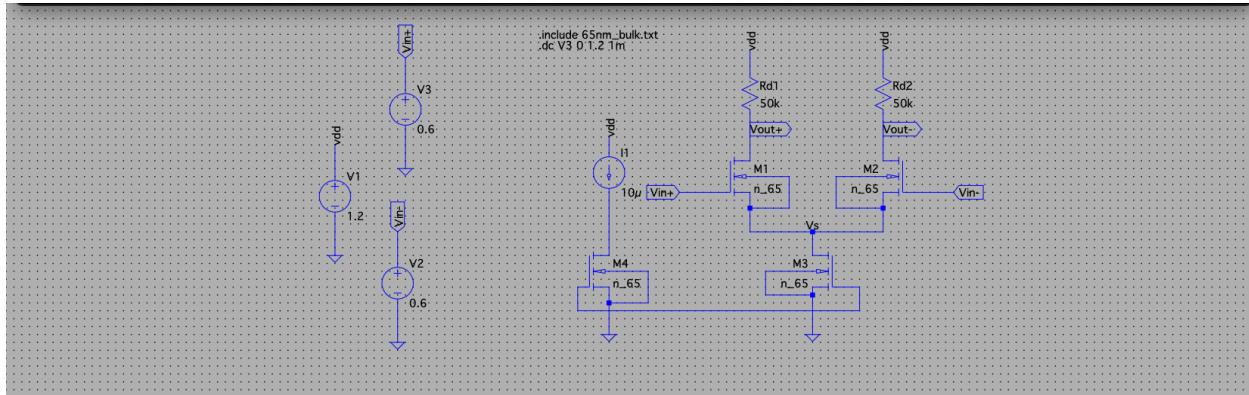a.i)Fix $V_{in-}=0.6V$,sweep V_{in+} from 0 to $V_{DD}(1.2V)$.obtain the plot for $V_{out}(-/+)$ and V_s .





Vout-(blue) , Vout+(green) and Vs(red).



Assignment 5: Differential amplifier

a.ii) Apply a fully differential signal $V_{int-} = -1\text{mV}$ p-p and $V_{int+} = 1\text{mV}$ p-p with common mode DC= 0.6V .Obtain output plots.

Circuit Diagram:

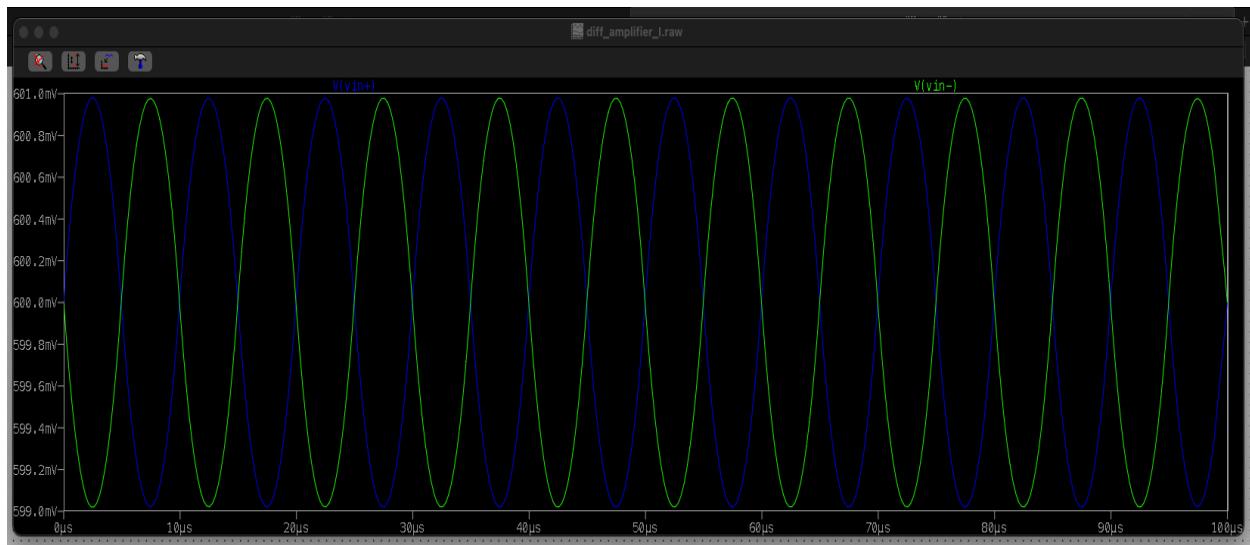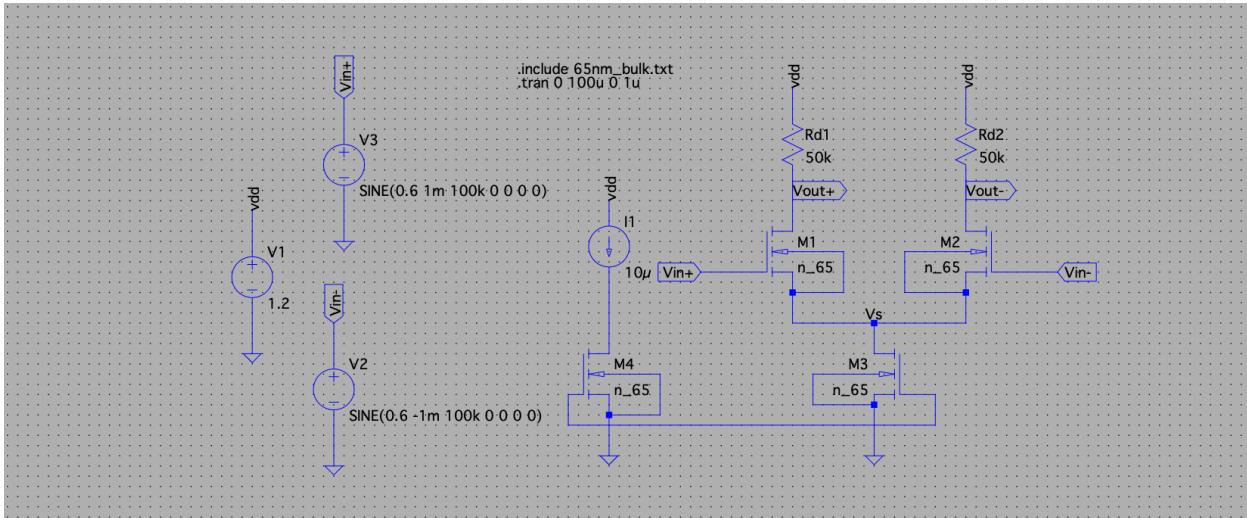

V_{in-} (green) and V_{in+} (blue)

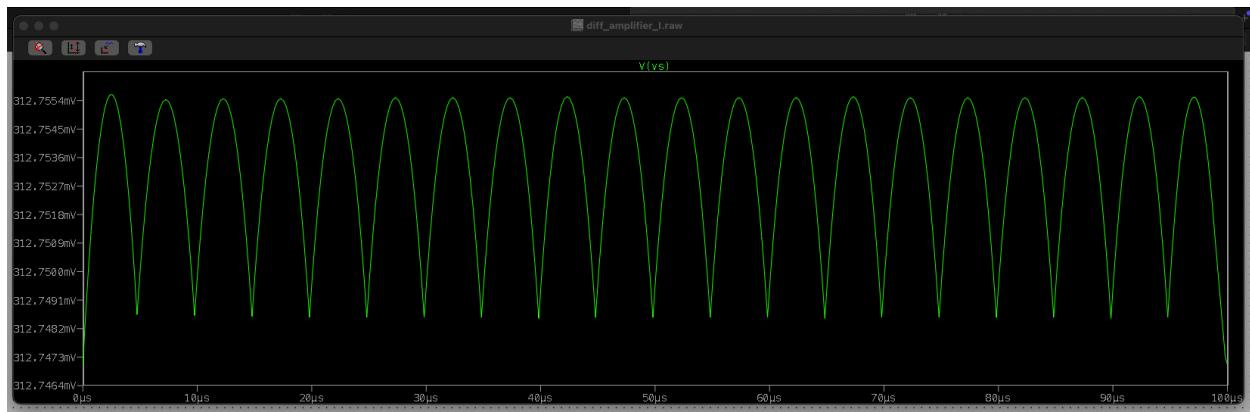
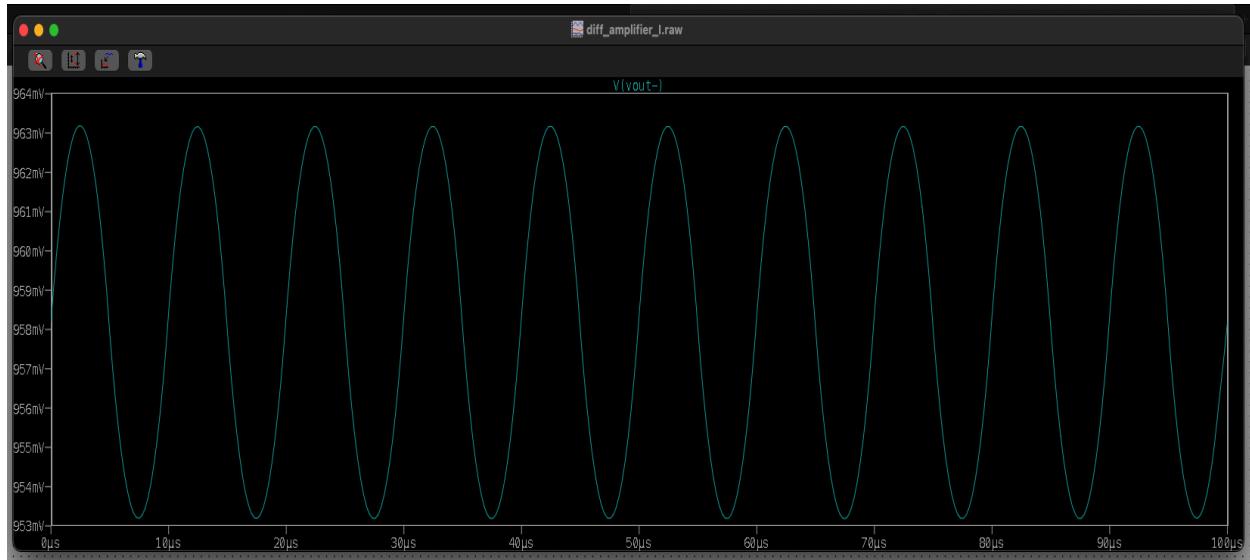


Vout-(red),Vout+(peacock green) and Vs(green)


Assignment 5: Differential amplifier

a.iii) Apply a common-mode sine signal of magnitude 10mV p-p with common mode DC =0.6V ,obtain the common mode output signal.

Circuit Diagram:

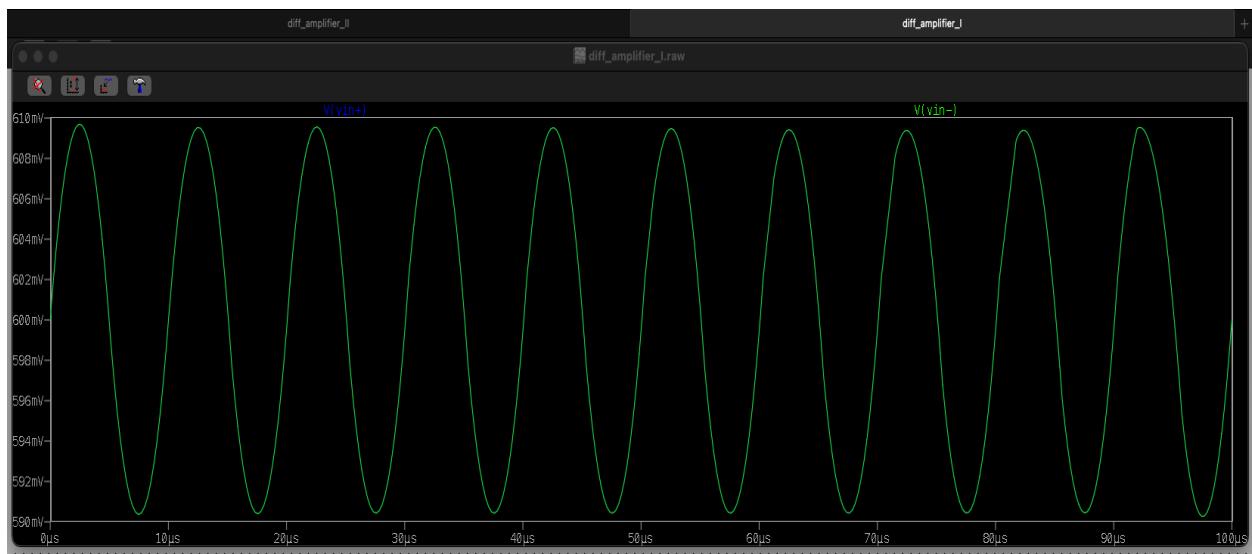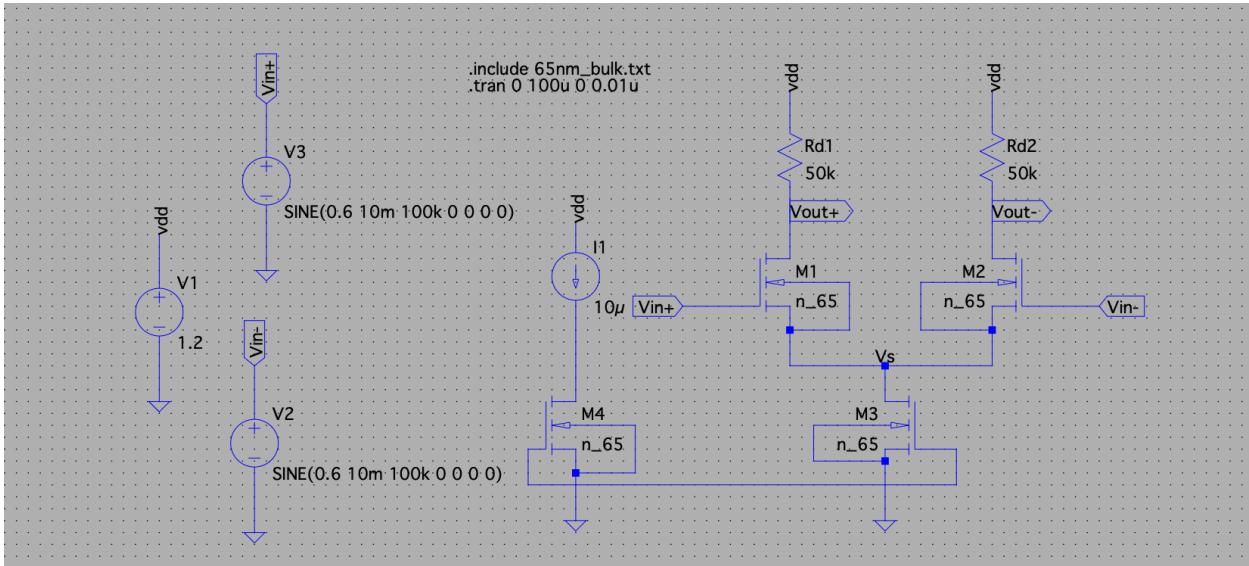

$V_{in}(+/-) \sim> \text{same plot.}$


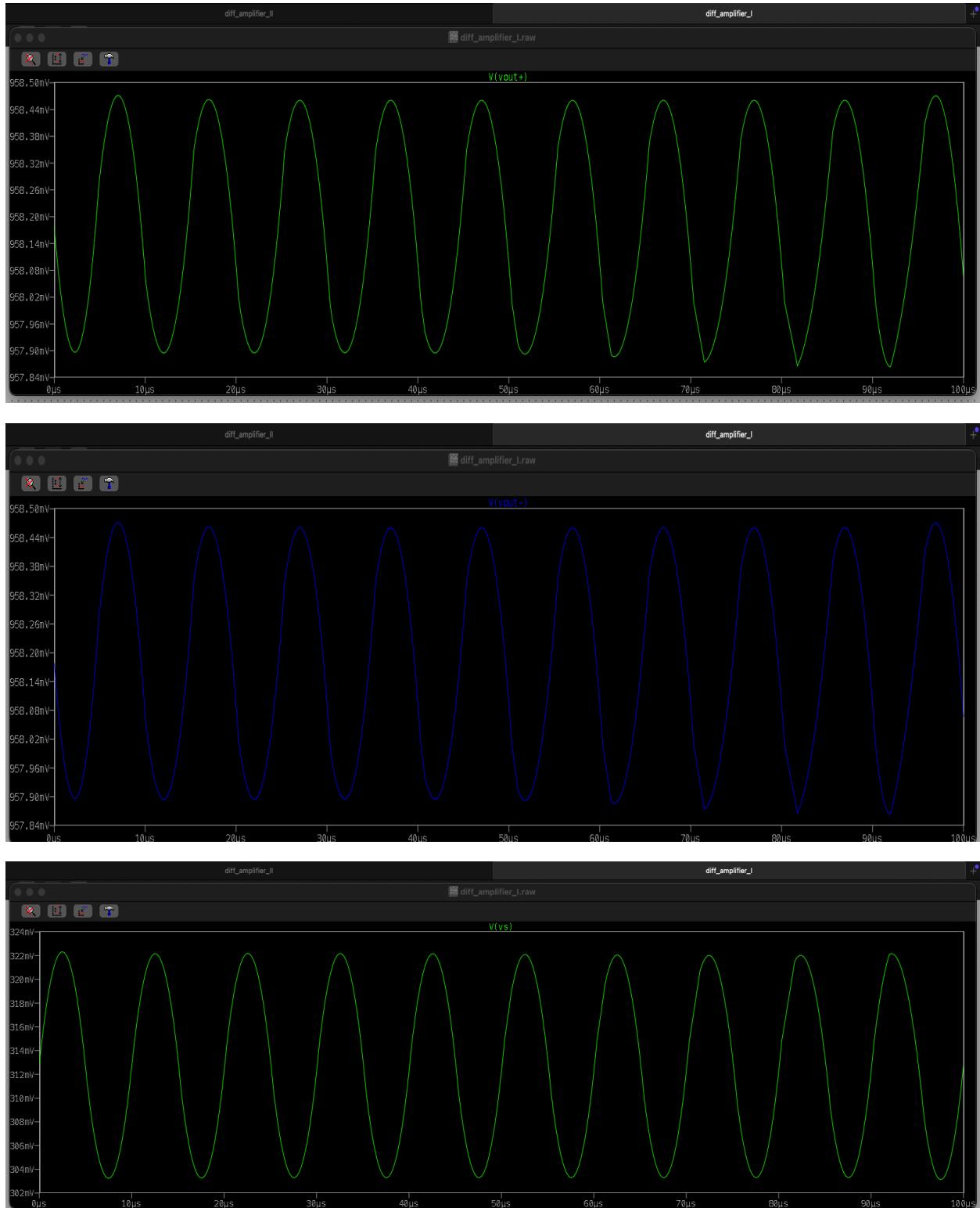


V_{out-} (green), V_{out+} (blue) and V_s (green)

Assignment 5: Differential amplifier


a.iv) Increase the gain of differential amplifier by 2x (with appropriate changes).

Circuit Diagram:

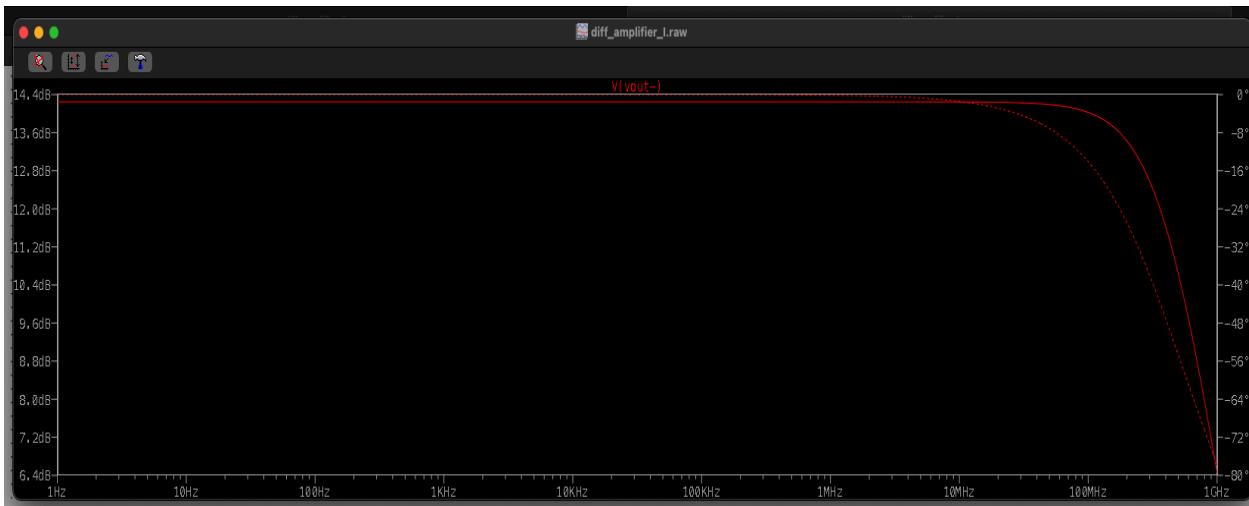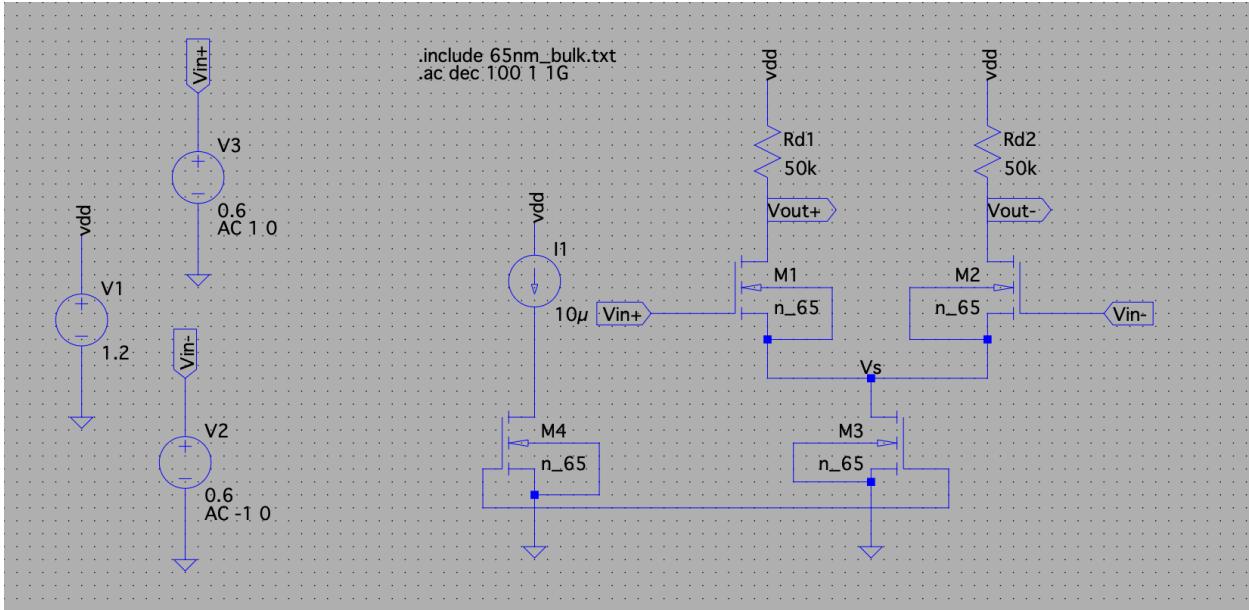

Gain(dB) ~ 14.2 dB.

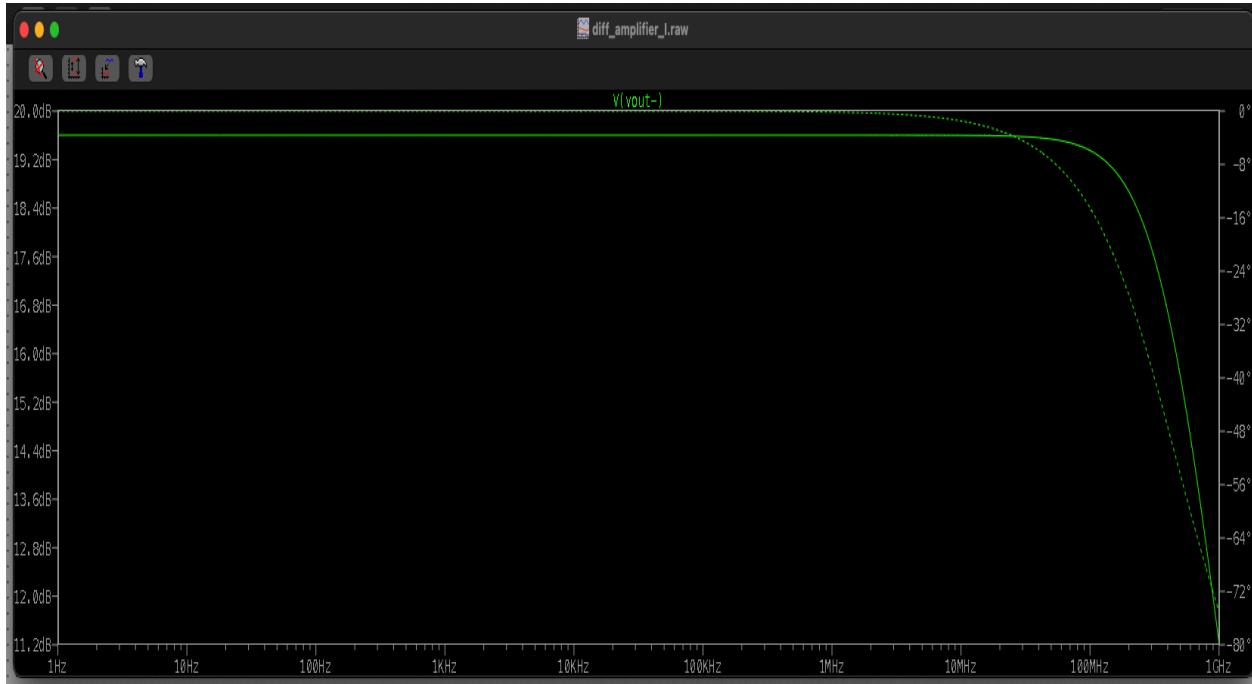For gain (~2x), we change the width of M3 by twice (i.e new width = 40um)




Gain(dB) ~ 19.52 dB.

Assignment 5: Differential amplifier

Part B:

- Circuit Diagram:

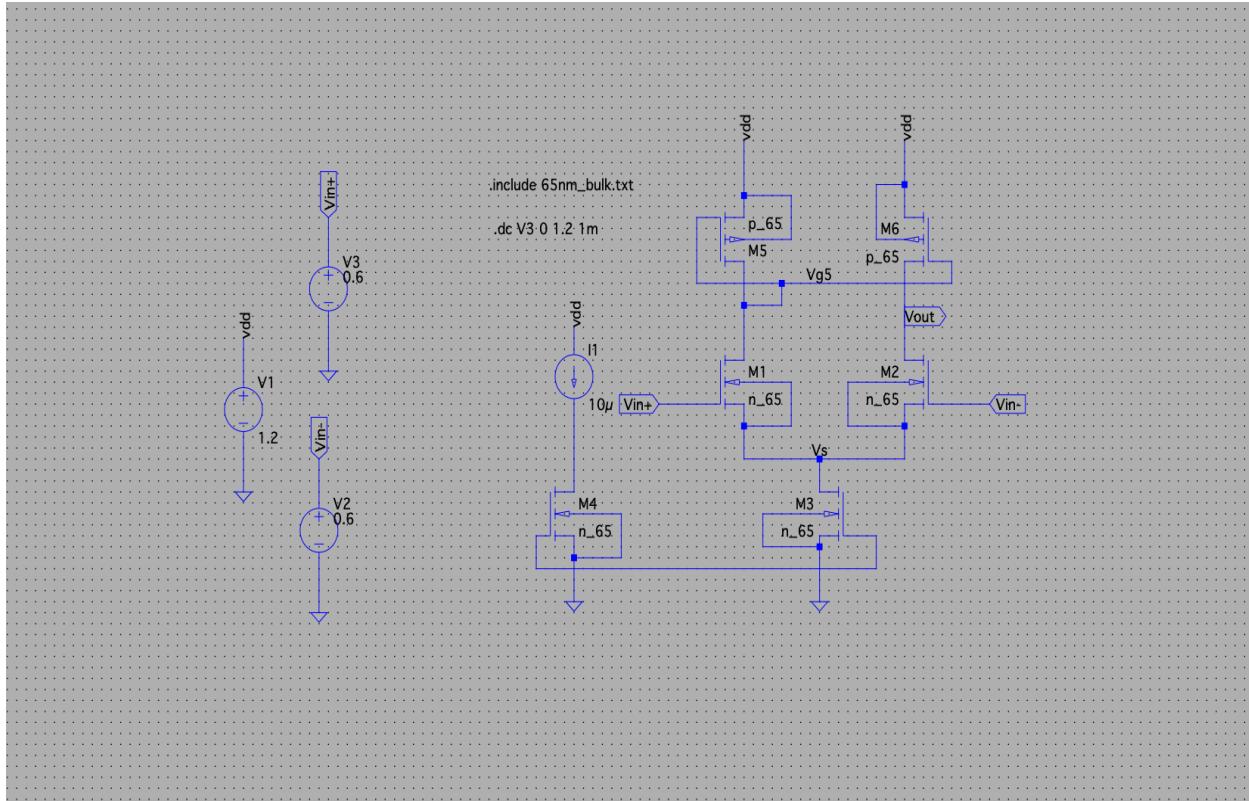

W/L ratios of different transistors used :


$M_1 = M_2 = 10\text{um}/180\text{nm}$

$M_3 = M_4 = 20\text{um}/300\text{nm}$

$M_5 = M_6 = 5\text{um} / 180\text{nm}$

Assignment 5: Differential amplifier

b.i) Find the ICMR using DC sweep.

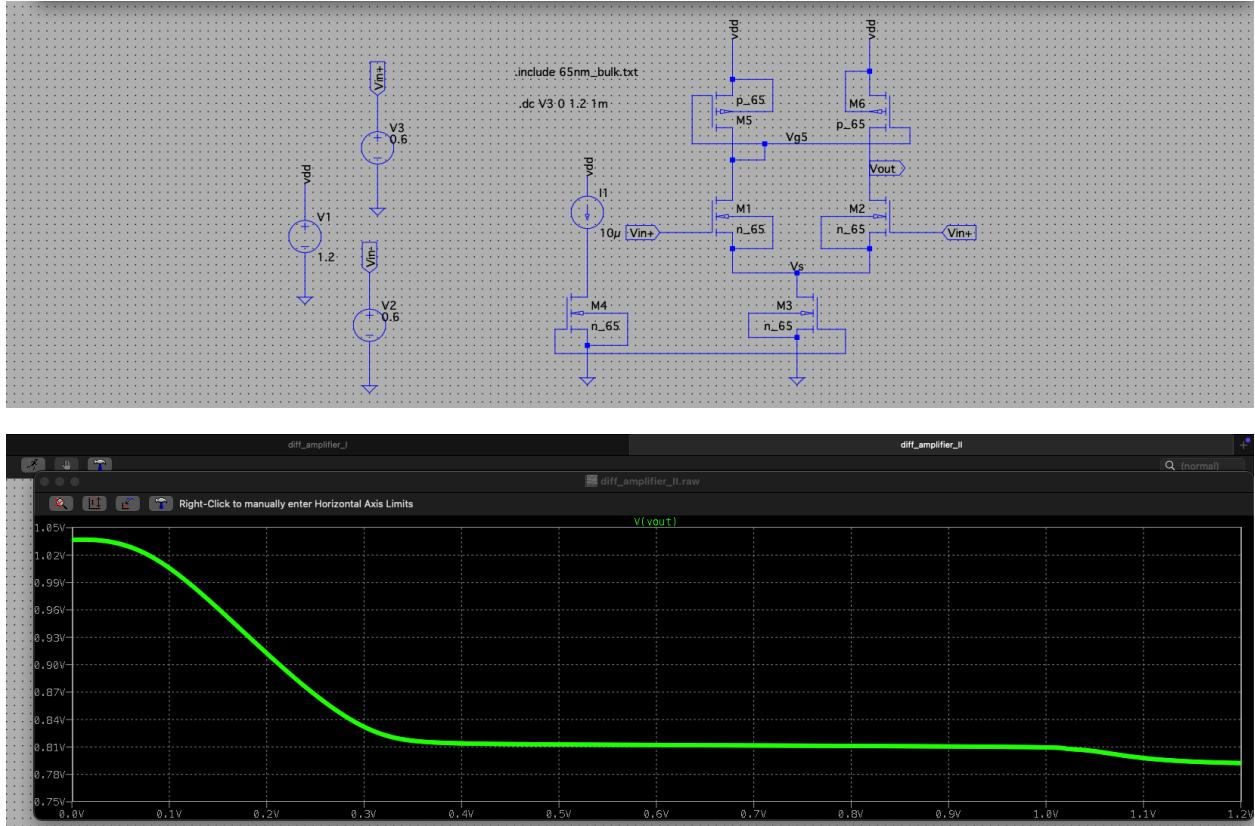


ICMR range $\sim(0.100 \text{ V} - 0.300 \text{ V})$.

Assignment 5: Differential amplifier

b.ii) For $V_{in_DC}=0.6$ V, find the A_{diff} and A_{cm} using frequency response (AC analysis). Validate using transient response and also at V_{gs} .


- Circuit Diagram:

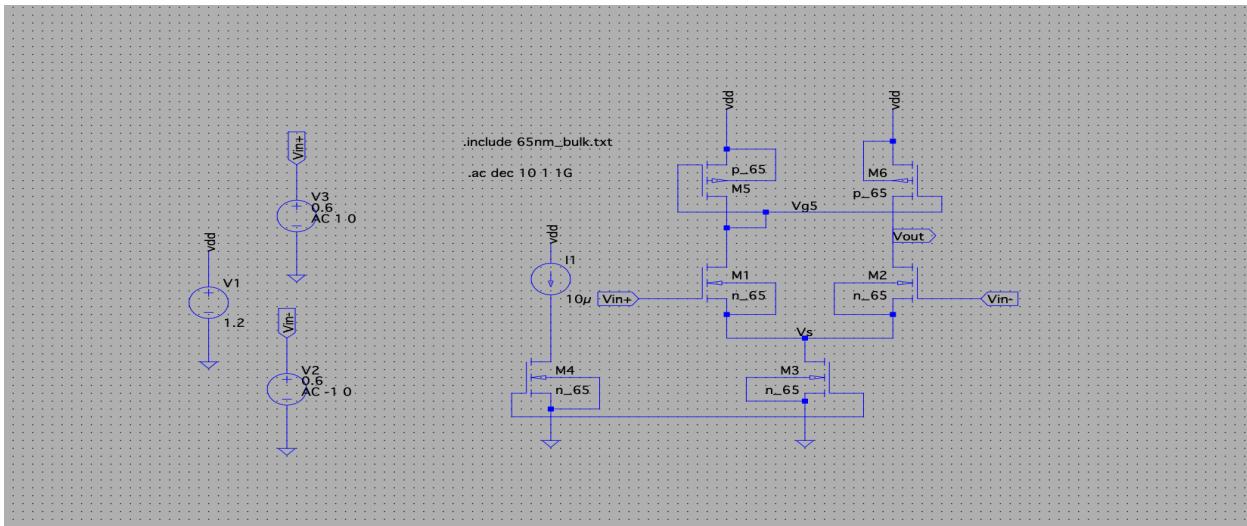

$\text{Gain(Adiff)} \sim 42.95 \text{ dB i.e } (V_{out} / V_{in}) = 140.44$

Assignment 5: Differential amplifier

Acm:

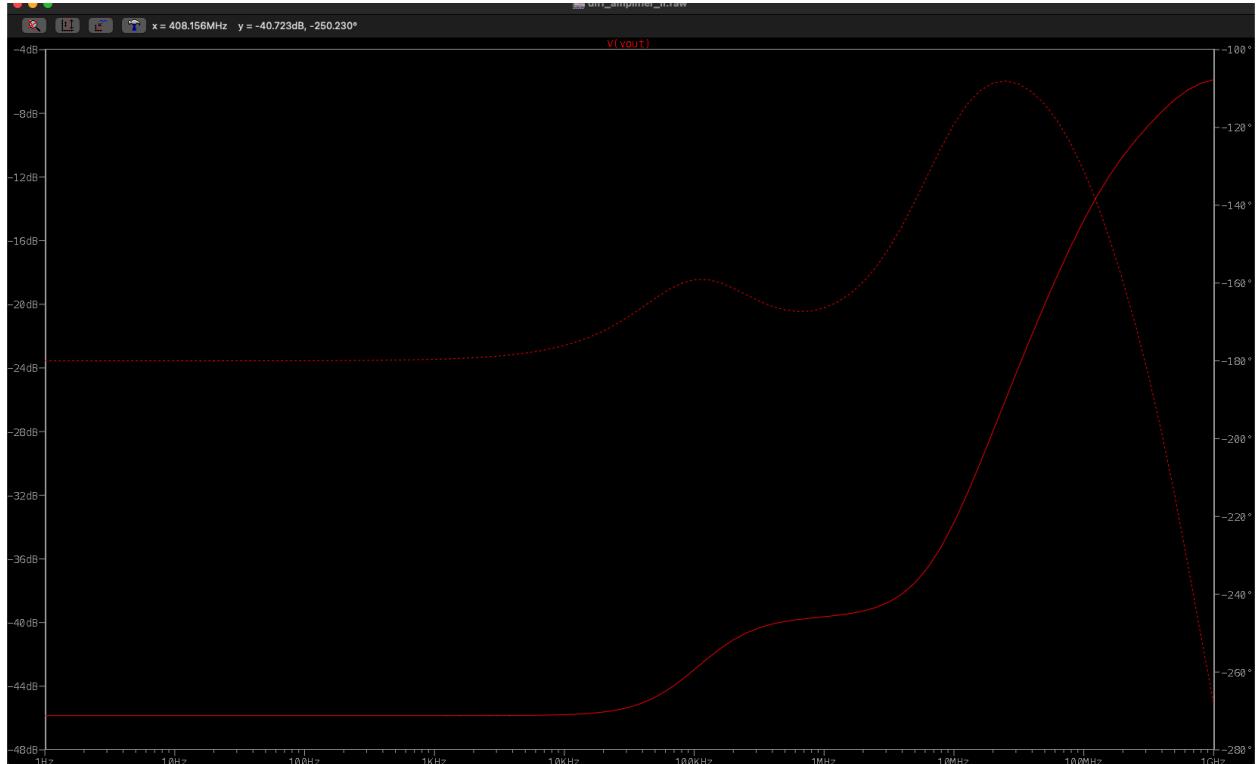


Gain(Acm)~ -46dB (for Frequency range - 1 Hz to 10k Hz) and

Gain (Acm) = -43 dB at 100k Hz i.e
 $V_{out}/V_{in}=0.0071$.

Assignment 5: Differential amplifier

- Transient response(at 100k frequency):

For common mode gain:

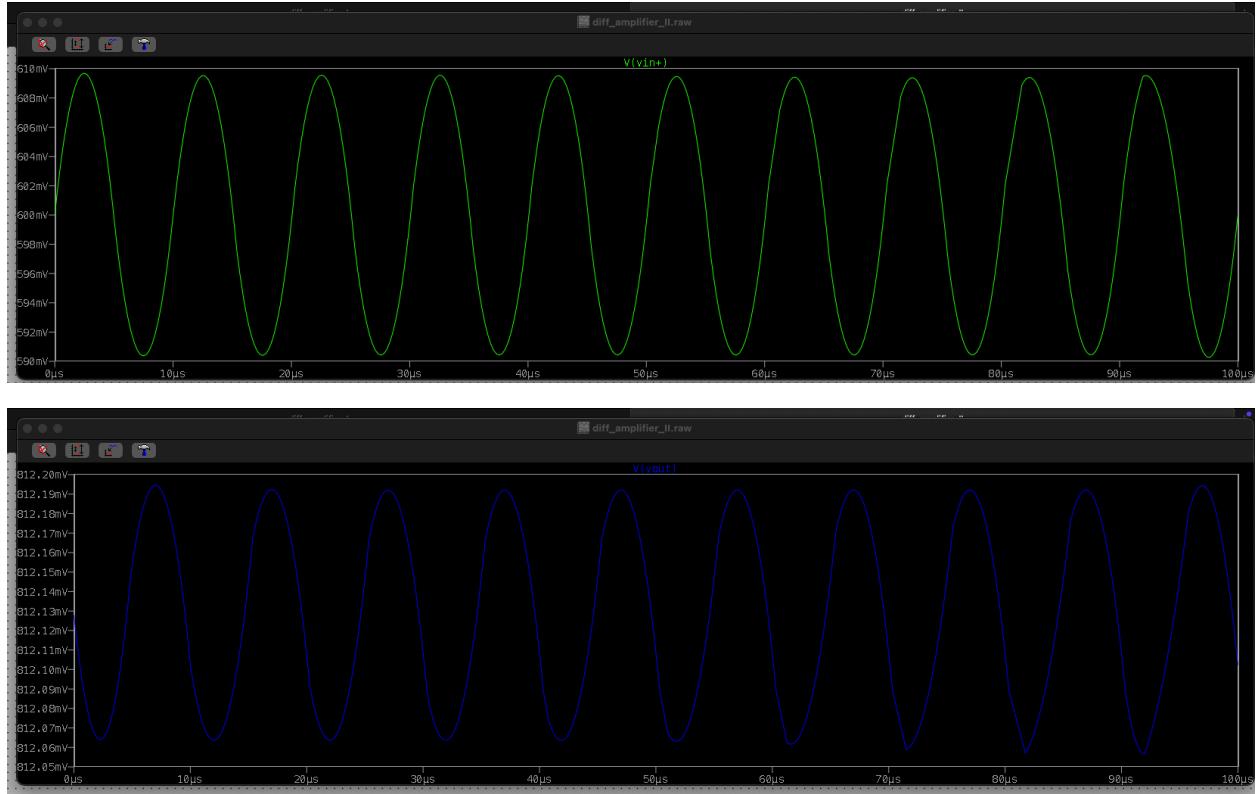

Hence , $V_{in}(p-p) = 20mV$.


$V_{out}(p-p) = 0.130mV$.

Then , $\text{Gain}(V/V) = .0065$, i.e -43.74dB which is nearly equal to that of AC analysis i.e -43 dB.

Assignment 5: Differential amplifier

- Transient response(at 100k frequency):

For differential gain:

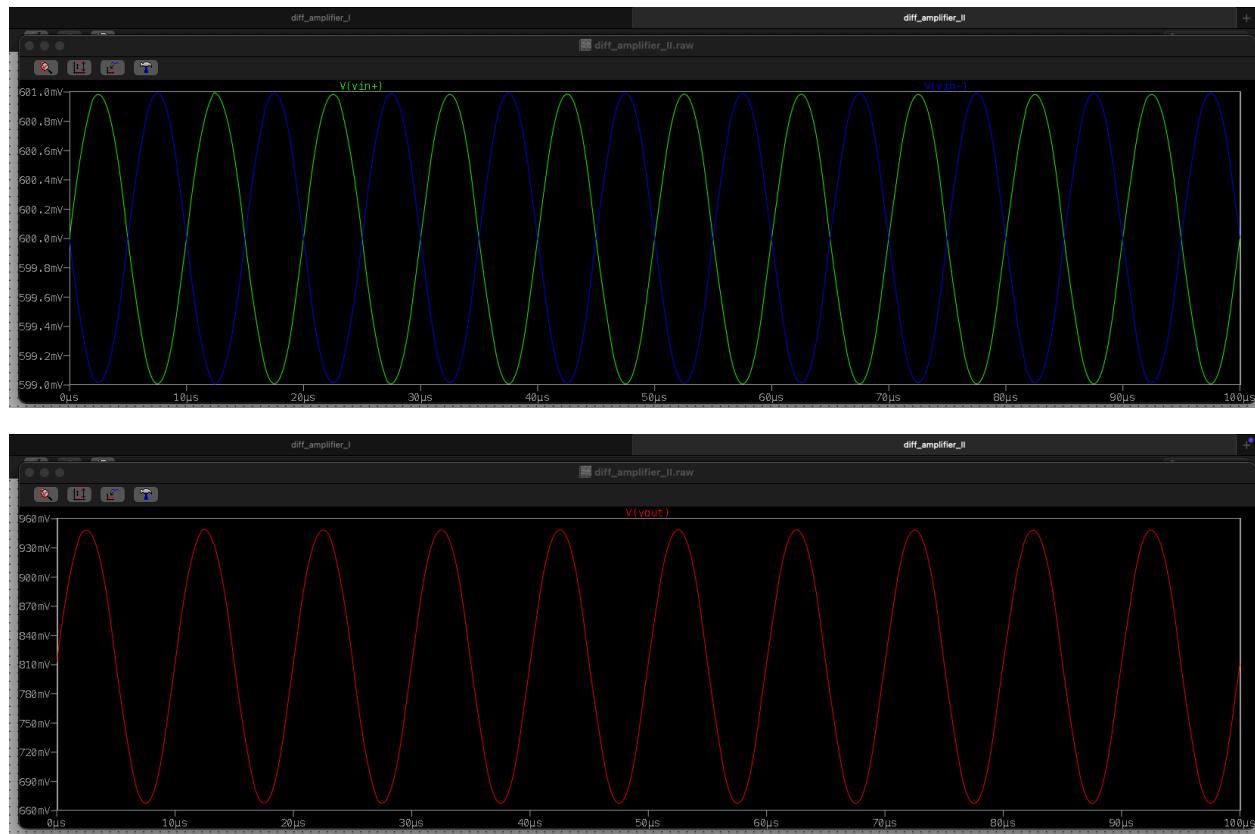

Hence , $V_{in}(p-p) = 2mV$.

$V_{out}(p-p) = 284mV$.


Then , $\text{Gain}(V/V) = 142$, i.e 43.04dB which is nearly equal to that of AC analysis i.e 42.95dB.

Assignment 5: Differential amplifier

- Transient response(at 100k frequency):

Vg5:

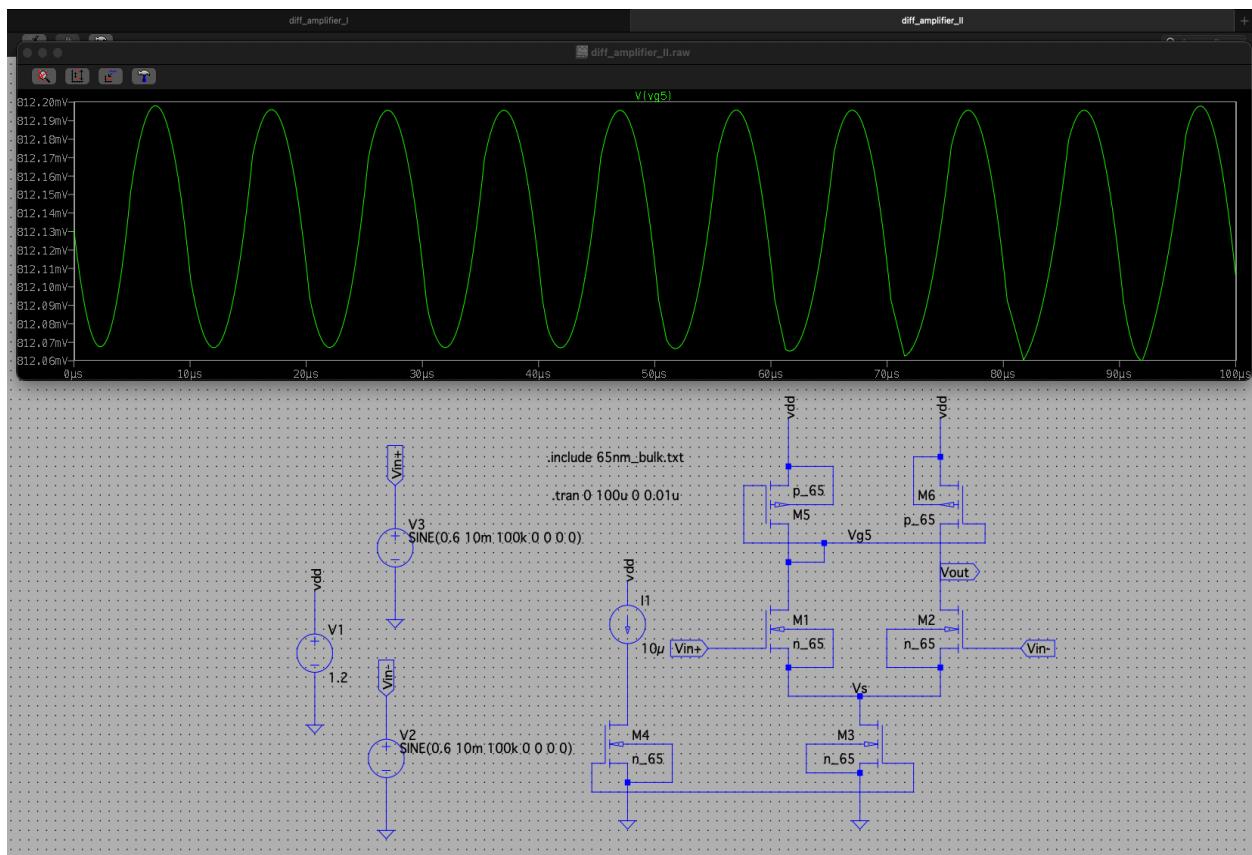(common mode response at Vin (p-p) =20mV).




$V_{g5}(p-p) = 0.13mV$.

Assignment 5: Differential amplifier

- Transient response(at 100k frequency):

Vg5:

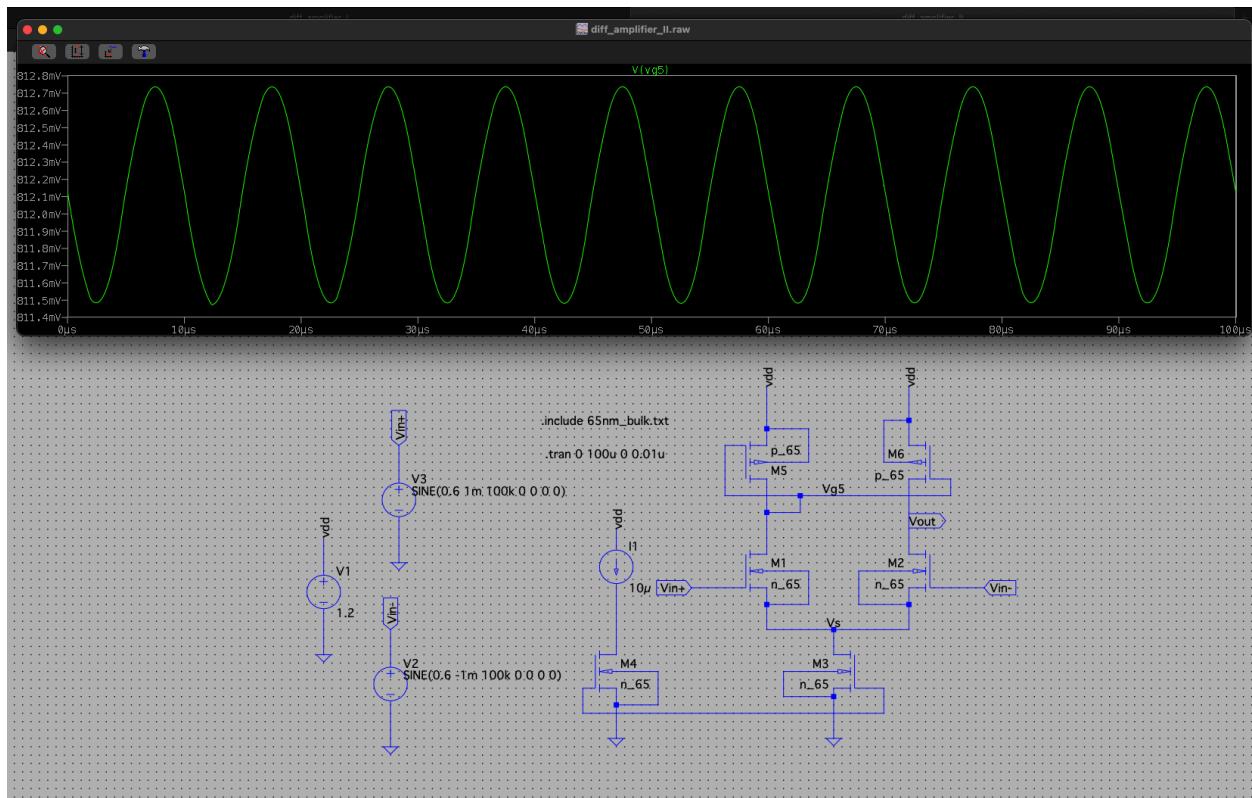(differential response at Vin (p-p) =2mV).






$$V_{g5}(p-p) = 1.2 \text{ mV.}$$

Assignment 5: Differential amplifier

b.iii) Increase the Adiff by 2x and reduce Acm by 2x using appropriate modifications.


- Circuit Diagram:

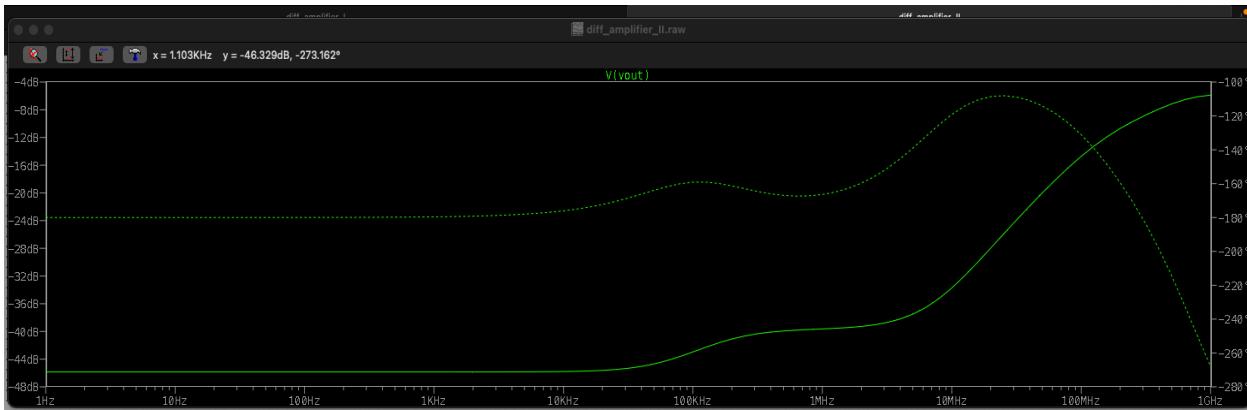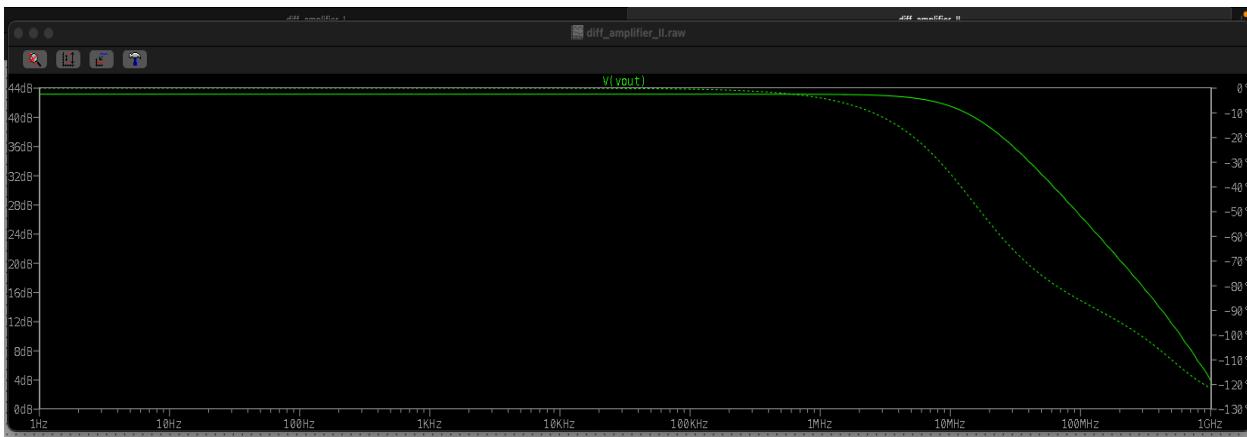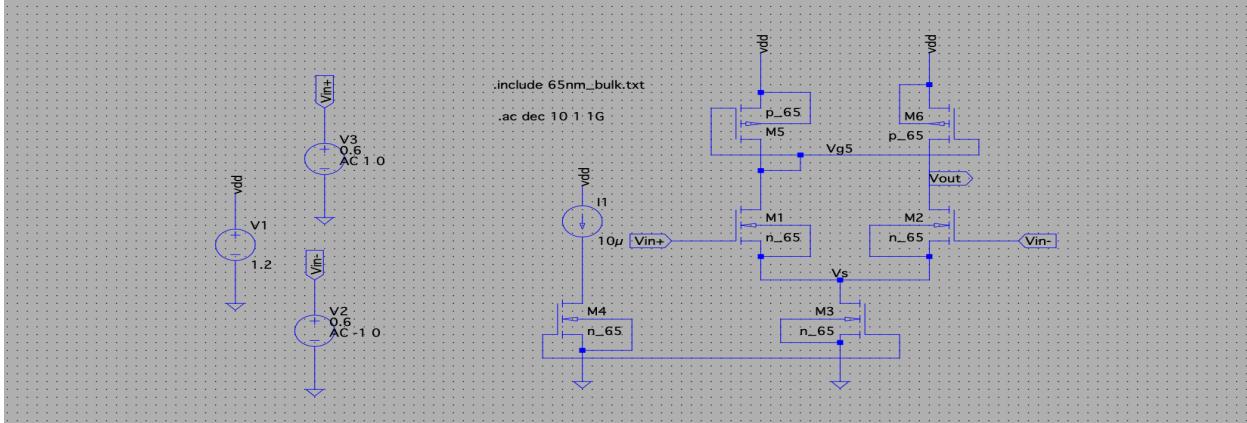

$$A_{cm} = -46.5 \text{ dB} \quad \text{and} \quad A_{diff} = 43.45 \text{ dB}$$

Assignment 5: Differential amplifier

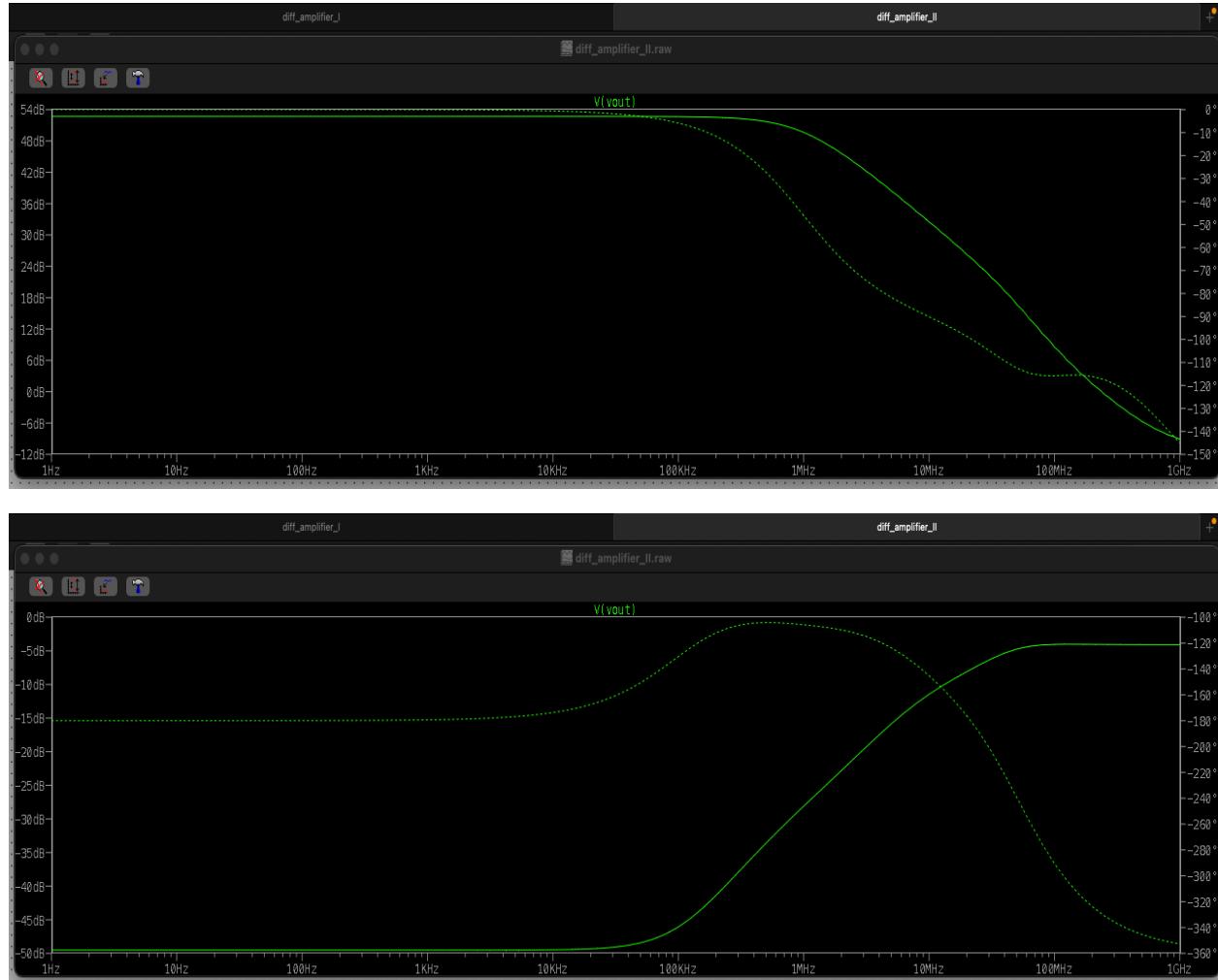- After changing W/L parameters of all transistors in the circuit by 5x.





Now ,the new A_{cm} value is -49.92dB and the new A_{diff} value is 53.25dB which is nearly an increase of 6dB in the A_{diff} value which is equivalent to 2x gain. And also A_{cm} decreases by nearly 4dB which is also nearly equivalent to decrease in gain by 2x.

Assignment 5: Differential amplifier

b.iv) Connect the diffamp in unity gain configuration and obtain Vout vs Vin curve using DC sweep.

Circuit Diagram:

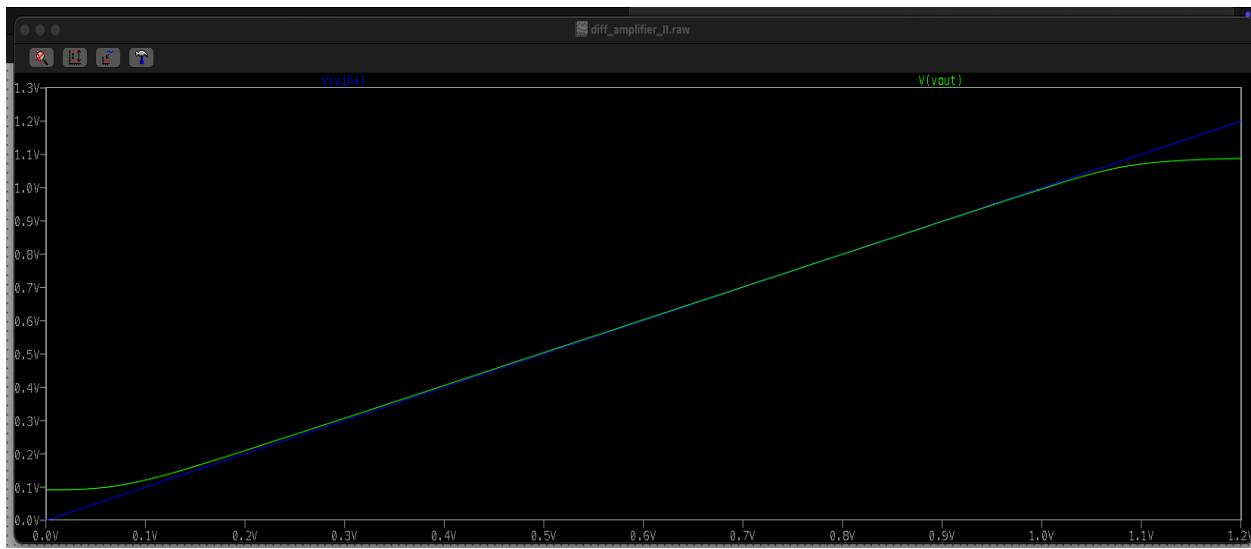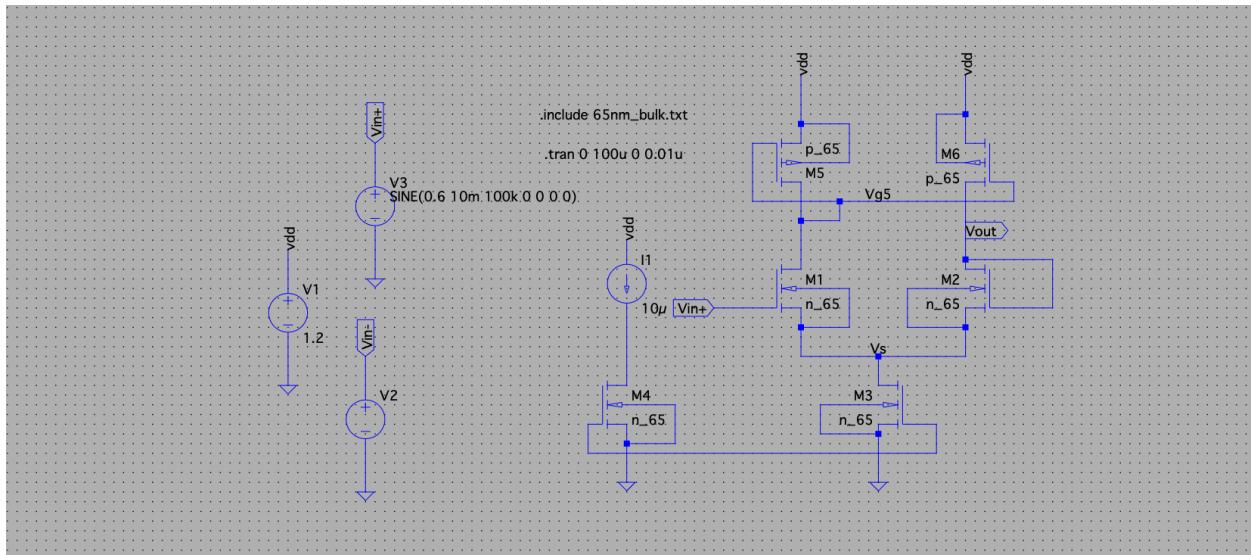

V_{in} (blue) and V_{out} (green).

